

No. of the panel:


$R_1 =$

$R_2 =$

$R_3 =$

No. of the source:

measured emf:  $\varepsilon =$

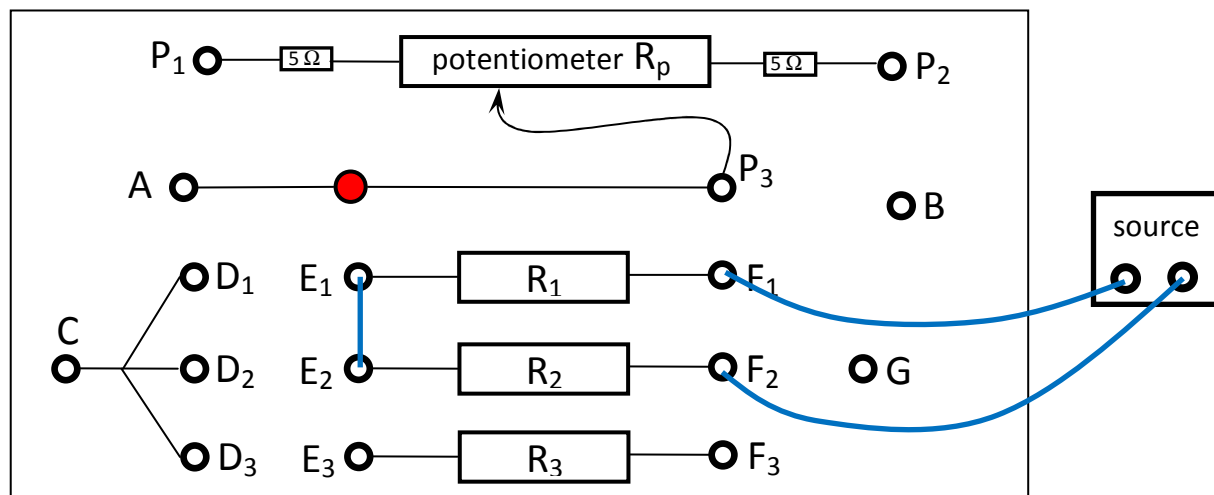

Draw the circuit diagram:


Connect the voltmeter between the points	measured voltage	resistance between the points	calculated current
$E_1$ and $F_1$	$V_{E_1F_1} =$		
$E_1$ and $E_2$	$V_{E_1E_2} =$		
$E_2$ and $F_2$	$V_{E_2F_2} =$		
$F_1$ and $F_2$	$V_{F_1F_2} =$		
			average:

The sum of the voltages ..... and ..... equals the voltage .....

Terminal voltage of the source:  $V_T =$

Calculate the internal resistance of the source from the formula  $V_T = \varepsilon - R_i \cdot I$  using the average current:

$R_i =$

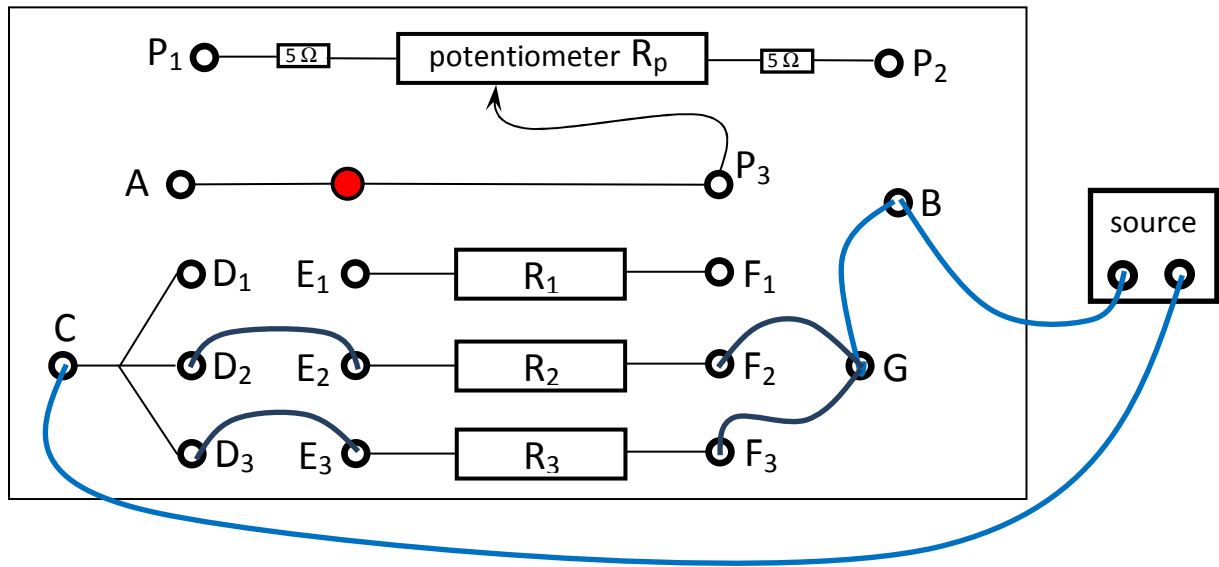

Draw the circuit diagram:

Remove the wire connecting  $D_2$  and  $E_2$   
 $D_3$  and  $E_3$   
 B and G and connect the ammeter in series between those points.

	measured current	resistance of the branch	calculated voltage
$D_2$ and $E_2$	$I_2 =$		
$D_3$ and $E_3$	$I_3 =$		
B and G	$I_s =$		

The sum of the currents ..... and ..... equals the current .....

Estimate the resistance of the ammeter:


calculate the resultant resistance of the circuit from  $R_2$ ,  $R_3$  and  $R_1$  :

$$R_{\text{res, c}} =$$

calculate the resultant resistance of the circuit from  $\epsilon$  and  $I_s$  :

$$R_{\text{res, m}} =$$
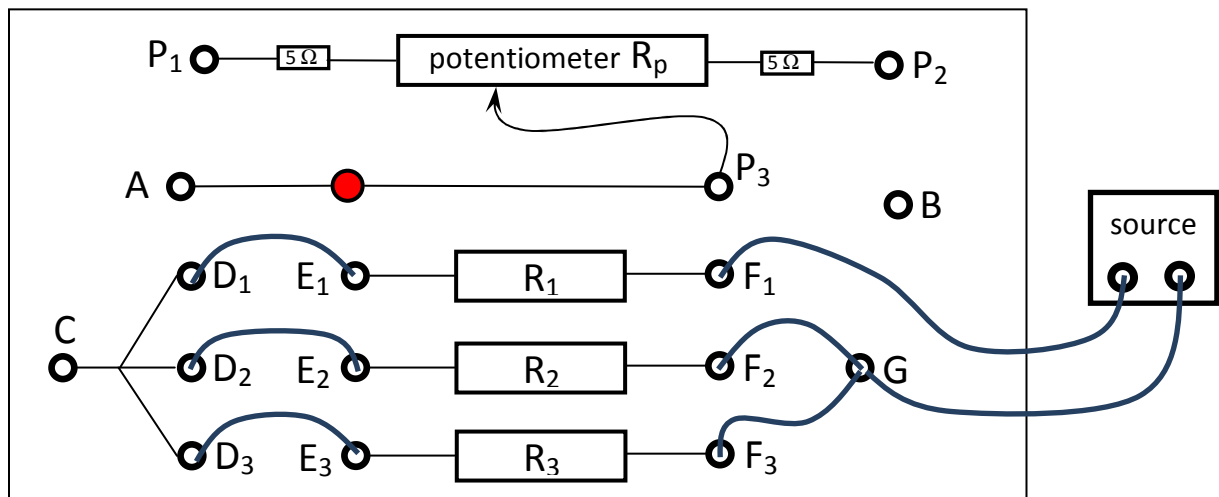
$$R_A = R_{\text{res, m}} - R_{\text{res, c}} \approx$$



Draw the circuit diagram:

Remove the wire connecting  $D_1$  and  $E_1$

$D_2$  and  $E_2$

$D_3$  and  $E_3$  and connect the **ammeter** in series between those points.

	measured current	resistance	calculated voltage
$D_1$ and $E_1$	$I_1 =$		
$D_2$ and $E_2$	$I_2 =$		
$D_3$ and $E_3$	$I_3 =$		

The sum of the currents ..... and ..... equals the current .....


The voltages ..... and ..... are equal.

Connect the <b>voltmeter</b> between	measured voltage	resistance	calculated current
$E_1$ and $F_1$	$V_{E1F1} =$		
$E_2$ and $F_2$	$V_{E2F2} =$		
$E_3$ and $F_3$	$V_{E3F3} =$		
$F_1$ and $G$	$V_{F1G} =$		

The voltages ..... and ..... are equal.

The sum of the voltages ..... and ..... equals the voltage .....

The currents ..... and ..... are equal.

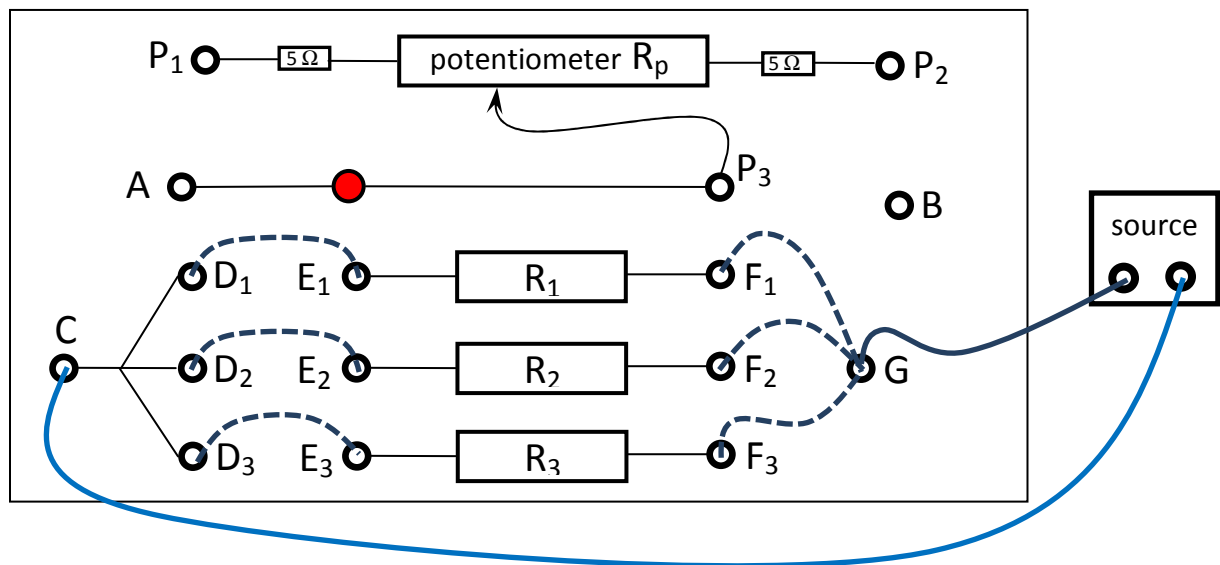

Measure the voltage between the points C and G.


resistances connected	resistance of the load $R_L$	measured voltage $V_T$	$V_T / (\varepsilon - V_T)$

Plot  $V_T / (\varepsilon - V_T)$  against  $R_L$  and calculate  $R_i$  from the slope:

$$V_T = \varepsilon - I \cdot R_i \quad \text{and} \quad I = \varepsilon / (R_L + R_i) \quad \rightarrow \quad V_T = \varepsilon \cdot R_L / (R_L + R_i) \quad \text{and} \quad \varepsilon - V_T = \varepsilon \cdot R_i / (R_L + R_i)$$

$$\rightarrow V_T / (\varepsilon - V_T) = R_L / R_i = (1/R_i) \cdot R_L$$

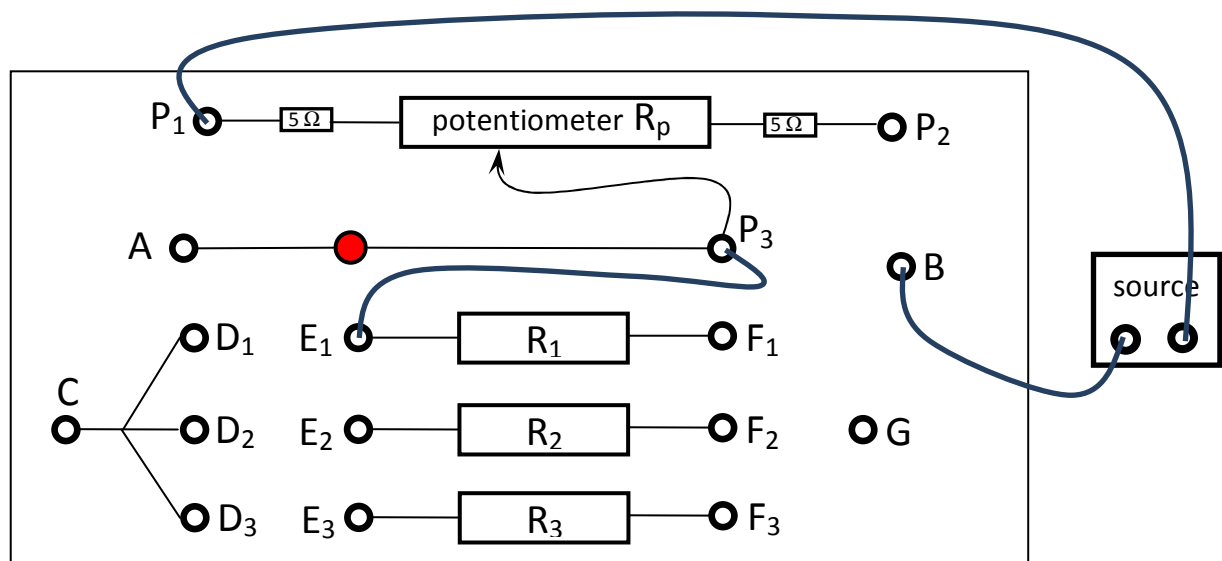Measure the resistance between  $P_1$  and  $P_2$ :  $R_{P_1P_2} =$   
 The resistance of the potentiometer:  $R_p = R_{P_1P_2} - 10 =$



Connect the ammeter between the points  $F_1$  and  $B$ .

Draw the circuit diagram:

Measure the maximum and the minimum value of the current:

$I_{\max,m} =$


$I_{\min,m} =$

Calculate the maximum and the minimum value of the current:

$I_{\max,c} = \varepsilon / (R_i + R_1 + R_A) =$

$I_{\min,c} = \varepsilon / (R_i + R_1 + R_A + R_p) =$

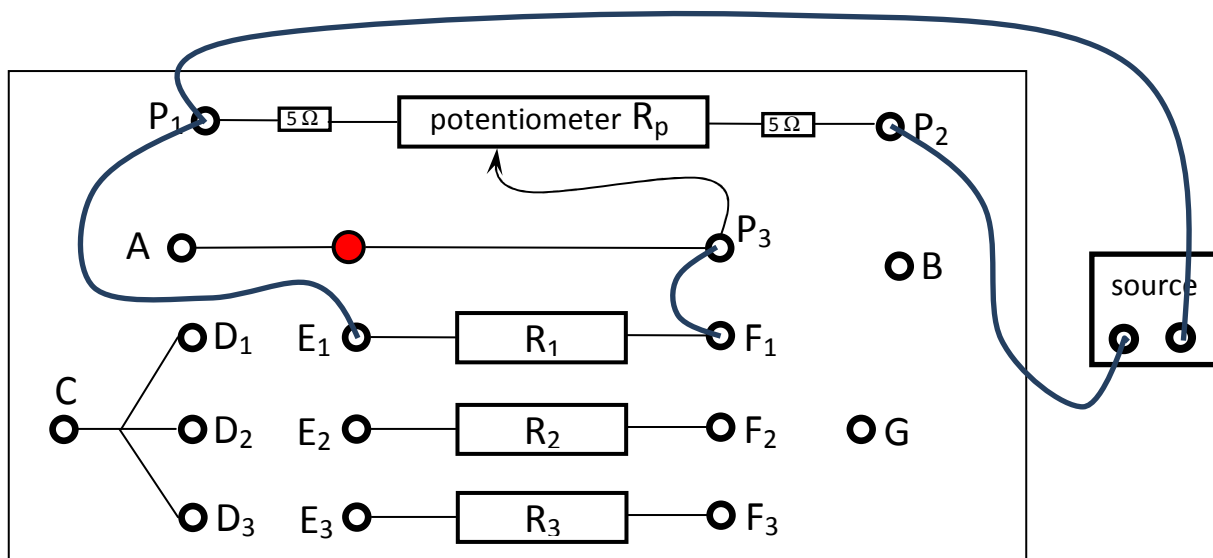Deviation of the measured and calculated values:



Connect the voltmeter between the points E<sub>1</sub> and F<sub>1</sub>.

Draw the circuit diagram:

Measure the maximum and the minimum value of the voltage:

$V_{\max} =$

$V_{\min} =$